

# Circuit Symbols




Wire




Button cell battery



Resistor

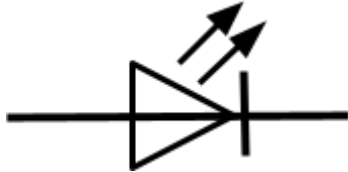

LED bulb

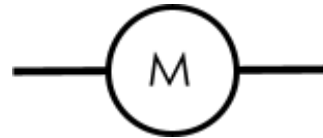

Motor




Push-to-break switch  
(Turns circuit off)



Push-to-make switch  
(Turns circuit on)

Example circuit:

Draw your circuit here:

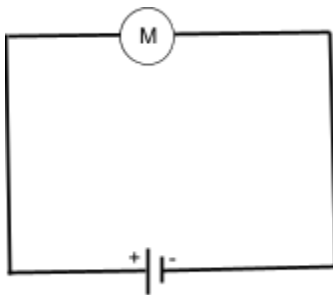

What symbols do you see here?